

## Modifying Start Convert Pulses Using Commercially Available Devices ADC-AN-07


by Tony Keirouz

This application note provides DATEL's sampling analog-to-digital (A/D) converter customers with two methods of adjusting the start convert pulse width.

The start convert input pulse is very critical to the operation of a sampling analog-to-digital (A/D) converter because it directly controls some of the internal timing of the device. To assure proper operation, a thorough study and clear understanding of the device's characteristics is essential.

Before discussing how to adjust the pulse width, let's explore just how critical the accuracy of a trigger pulse is to the operation of a sampling A/D converter. In most cases, any variation from the specified pulse width will lead to malfunctioning of the device.

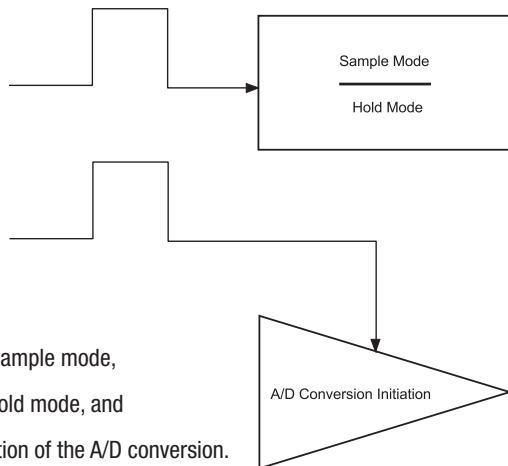Historically, design engineers had to carefully control the timing of three different functions:



- 1 – The sample mode,
- 2 – the hold mode, and
- 3 – initiation of the A/D conversion.

This often meant that the user had to generate at least two pulses.

### New Technology Provides an Answer.

The last few years have seen a growing popularity of sampling A/D's. Their availability is largely a response to the demand for higher conversion speeds and resolutions.

These devices incorporate internal gate array and logic circuitry, providing the necessary timing sequences which are triggered off a single external start convert pulse. Users, in most cases, only have to provide one pulse to control all operations.

As an example, DATEL's ADS-117 specifies a pulse width ( $t_w$ ) of 50 nanoseconds (30 nsec. minimum, 60 nsec. maximum) for proper operation at a sampling rate of 2 MHz. A timing diagram of the ideal situation would look like the one shown in Figure 1.

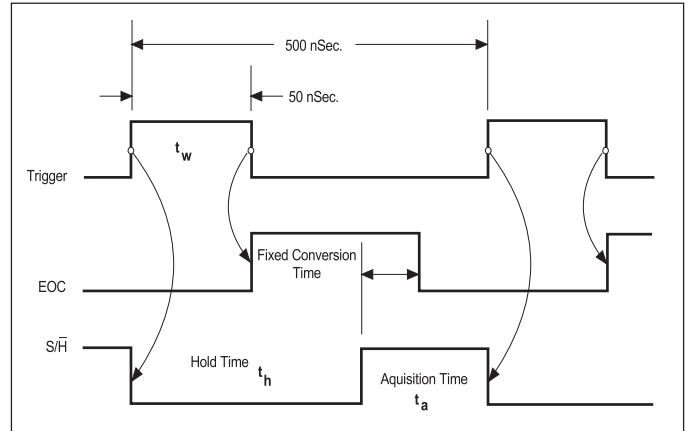


Figure 1. Accurate Trigger Pulse

### Effects of Changing the Pulse Width

#### With too short a pulse width...

If the pulse width of the trigger pulse is *shorter* than the recommended 30 nanoseconds, minimum, ( $t_w = 20$  ns), the design engineer would violate the *hold mode settling time*. This is the time from the hold command transition until the output of the sample-hold settles to within a specified accuracy.

$t_{h1} < t_h$  (hold mode settling time required)

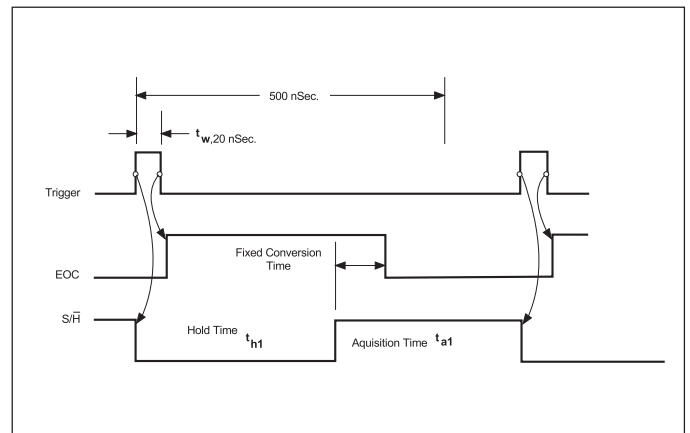


Figure 1a. Effects of a Short Trigger Pulse

#### With too long a pulse width...

Operating at the maximum speed with a *longer* than recommended trigger pulse, ( $t_w = 100$  ns), would violate the device's acquisition time specification, in addition to creating a droop concern.

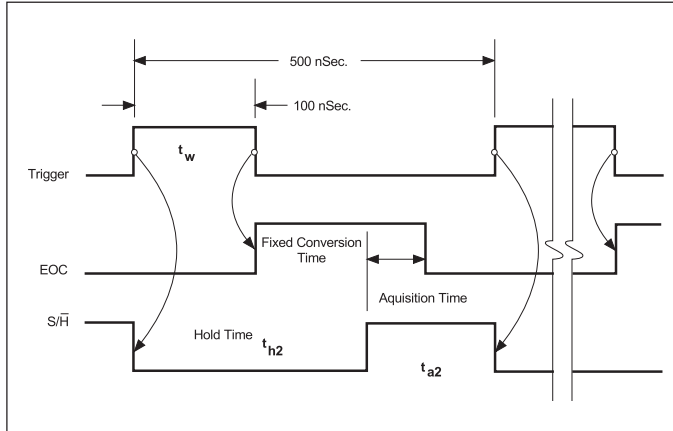


Figure 1b. Effects of a Long Trigger Pulse

In this example, the acquisition time ( $t_{a2}$ ) is smaller than the specified time ( $t_a$ ) needed for the hold capacitor of the sample/ hold to charge to a full scale voltage and then remain within a specified accuracy around the final value.

The following discussion explains only two of the many ways to adjust the pulse width of a digital signal.

Both circuit descriptions that follow assume that the period of the applied external clock ( $t_1$ ) is greater than the pulse-width being created ( $t_2$ ), as shown in Figure 2. In the example using a D-type flip-flop,  $t_1$  must be at least twice as large as  $t_2$ .

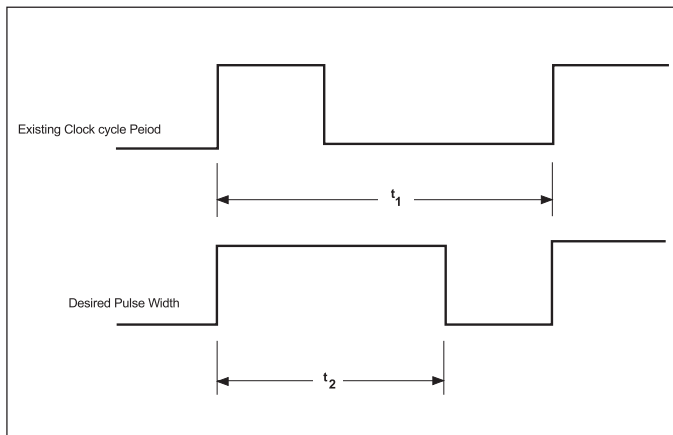


Figure 2. Pulse Width Relationships

## Creating an Accurate Pulse

### Option A – Using a D-Type Flip-Flop

As an intermediate device between the trigger pulse and the start convert input of the A/D converter, a D-type flip-flop with an external resistor and capacitor lets the design engineer vary the pulse width as required.

The flip-flop recommended is a D-type positive-edge-triggered Series 54ACT74 sold by National Semiconductor, Motorola, RCA, and other vendors. These devices have independent DATA, SET, RESET, and CLOCK inputs, with Q and  $\bar{Q}$  outputs. The logic level present at the data input is transferred to the output during the positive-going transition of the clock pulse (CP). SET and RESET are independent of the clock and are active low inputs.

Note: Since FF2 is not used, connect  $\bar{2R}$  and  $\bar{2S}$  high; ground 2CP and 2D.

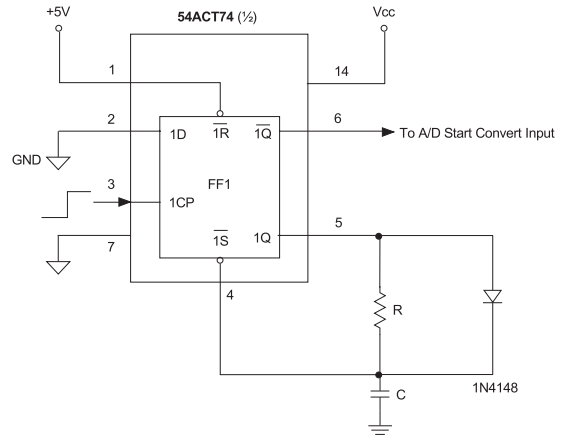


Figure 3. Connections for 54ACT74 Dual Flip-Flop

## TRUTH TABLE

Inputs				Outputs	
$\bar{S}$	$\bar{R}$	CP	D	Q	$\bar{Q}$
L	H	X	X	H	L
H	L	X	X	L	H
L	L	X	X	H*	H*
H	H		H	H	L
H	H		L	L	H
H	H	L	X	Q0	$\bar{Q}0$

H = High level (steady state)

L = Low level (steady state)

X = Don't care

= Transition from low to high level.

Q0 = the level of Q before indicated input conditions.

\*This configuration is nonstable, that is, it will not persist when set and reset inputs return to their inactive (high) level.

## Circuit Description

Adding an external resistor and capacitor to the flip-flop, as shown in Figure 3, creates a delay at the SET input. This time delay corresponds to the pulse width ( $t_2$ ) of Q which is directly proportional to the resistor and capacitor values used ( $t_2 \approx R \times C$ ).

Preconditions: D is tied low,  $\bar{R}$  is tied high,  $\bar{S}$  is high initially. See Figure 3.

At the rising edge of the clock pulse,  $\bar{Q}$  goes high while Q goes low. This change forces  $\bar{S}$  to go low after the time delay ( $t_2$ ) caused by the resistor/capacitor circuit connected between Q and  $\bar{S}$ .

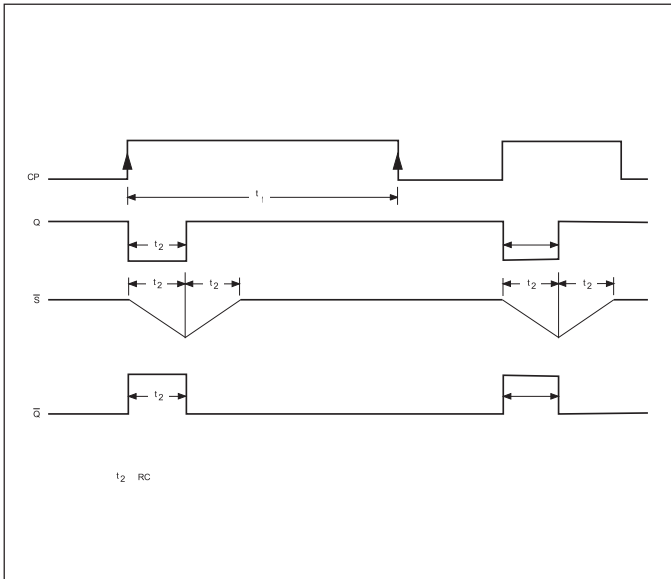


Figure 4. Input/Output Timing Relationships

Now  $\overline{SET}$  is low and  $\overline{RESET}$  is high, so automatically  $\overline{Q}$  goes low and Q goes high. This drives  $\overline{S}$  back to a high state after a similar time delay, completing the cycle.

This explains why  $t_i$  should be greater than  $2 \times t_2$ . If  $\overline{S}$  stays low, the flip-flop will not respond to a retriggered CP input. Adding a diode across R, also shown in Figure 3, speeds up the transition of  $\overline{S}$  from low to high, allowing a quicker retriggering of the clock input pulse.

The design engineer should test different values of R and C to get the exact pulse width required. For limitations and operating conditions of the 54ACT74, refer to the vendor's data sheet.

### Creating an Accurate Pulse

#### Option B – Using a Multivibrator

Another way of obtaining the required pulse width is by using a multivibrator. The multivibrator suggested is a Series '121' supplied by Motorola, National Semiconductor, Texas Instruments, and other vendors. A simple RC time constant determines the output pulse width. The RC circuit may consist of external components or an internal capacitor and an internal 2K ohm resistor. Figure 5 shows a typical connection scheme; for operating conditions of the '121,' refer to the vendor's data sheet.

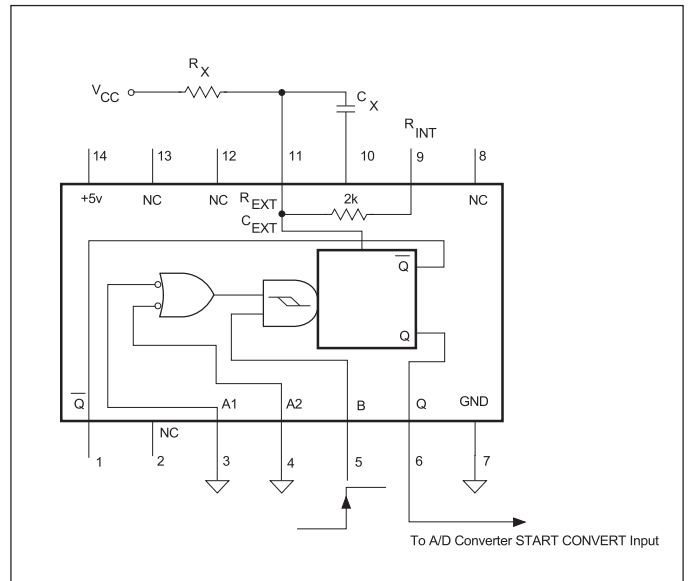


Figure 5. Typical Series '121' Connections for Pulse Generation

### FUNCTION TABLE

Inputs			Outputs	
A1	A2	B	Q	$\overline{Q}$
L	X	H	L	H
X	L	H	L	H
X	X	L	L	H
H	H	X	L	H
H		H		
	H	H		
	H	H		
L	X			
X	L			

The multivibrator should be set up as follows:

Inputs			Outputs	
A1	A2	B	Q	$\overline{Q}$
L	X			

## Circuit Description

The basic output pulse width is determined by using an external capacitor ( $C_X$ ) in conjunction with a resistor, as shown in Figure 5. The internal 2 k $\Omega$  resistor may be used instead of an external resistor ( $R$ ) by connecting RINT (pin 9) to  $V_{CC}$  (pin 14). The pulse width can vary from 30 nanoseconds to 28 seconds.

1. To determine the pulse width when  $C_X > 1000$  pF, refer to Figure 6.
2. For  $C < 1000$  pF, the output pulse width ( $t$ ) is determined as follows:

$$t_W = K \times R_X \times C_X$$

Where:

$R$  is in k $\Omega$

$C_X$  is in pF

$t_W$  is in nanoseconds

$K \approx 0.7$

**NOTE:** The "K" coefficient is not a constant, but varies as a function of the timing capacitor,  $C_X$ . Figure 7 details this characteristic.

 


Figure 6. Typical Output Pulse Width vs. External Timing Capacitance

 


Figure 7. "K" Coefficient